
Signal Generator & Function generator

■ Signal source

- **signal generator** – generates sine wave and optionally few others signal wave form : square ($\eta=50\%$), saw tooth, triangle (from original sin wave);
 - advantage: low THD for sine wave
 - disadvantage: limitation in other waveform generation;
- **function generator** – generates basically other waveform: square (variable η), triangle, etc.
 - **Direct analog synthesizer** generator (DAS) - Sine wave is obtained indirectly from triangle wave with sine shape circuit (analog generator);
 - **Direct digital synthesizer** generator (DDS) – the wave form is obtained by DAC conversion of signal digital samples;
 - advantage: many waveforms with variables parameters
 - disadvantage: significant THD for sine wave; limited high frequency signals (DDS)

EMI Ch 5 – Signal & Function Generator

■ Analog Signal source

- **RC oscillator signal generator**

- Low complexity (RC oscillator);
 - Very low TDH for sine wave;
 - Poor frequency stability and resolution;
 - Small frequency range (<500kHz)




- **Direct analog synthesizer (DAS)**

- High frequency stability (0.003ppm/ 24h)
 - Good frequency resolution ($\Delta f=0.01\text{Hz}$)
 - Large frequency range (0.1 – 500MHz)
 - Very high complexity and difficult adjustments (uses one quartz crystal and analog multipliers for frequency synthesis)



EMI Ch 5 – Signal & Function Generator

- **DAS Example – HP5100**

 


■ Low frequency function generators

- generate square waveform, triangle waveform (using RC integrator circuit), sine wave (conversion from triangle);
- advantages/disadvantages
 - low complexity;
 - AM modulation and other waveform generation possibility;
 - small frequency range (mHz – 1 MHz);
 - acceptable stability and frequency resolution;
 - poor THD for sine wave;

■ Hysteresis comparator


- component of oscillator

 

$$V_0 = +U_Z, v_i \downarrow, v_i < U_{P-} = -\frac{R_1}{R_2}U_Z \Rightarrow V_0 = -U_Z \text{ (blue)}$$


$$V_0 = -U_Z, v_i \uparrow, v_i > U_{P+} = \frac{R_1}{R_2}U_Z \Rightarrow V_0 = +U_Z \text{ (red)}$$
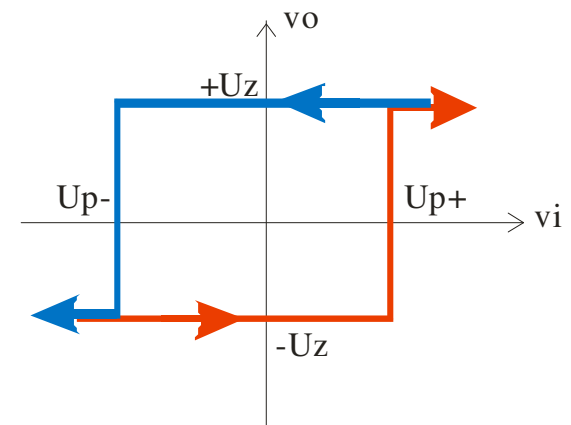
$$\Delta U_P = U_{P+} - U_{P-} = \frac{2R_1}{R_2}U_Z \text{ (trigger window)}$$



EMI Ch 5 – Signal & Function Generator

■ Low frequency function generator

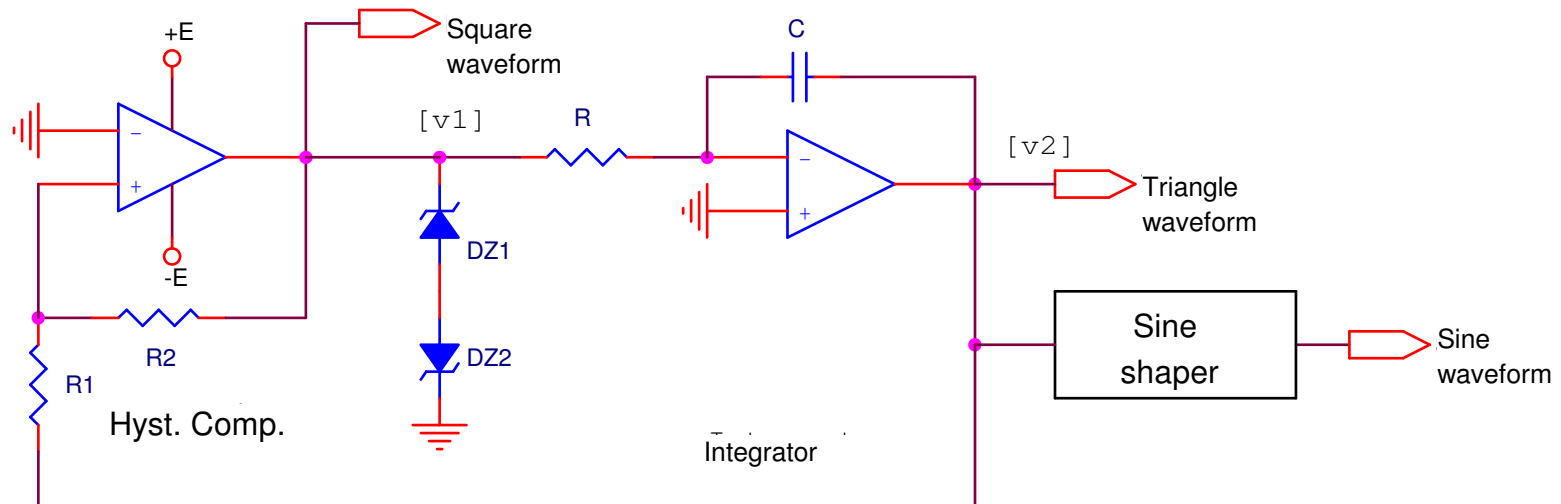


$t=0$, $v_1=+U_z$, $v_2=U_{p+}$ decreases

$t_1=RCR_1/R_2$, $T=4t_1$


Note: $R_1=R_2 \rightarrow U_p=U_z$

 advantage: same amplitude for square and triangle waveform



EMI Ch 5 – Signal & Function Generator

Low-medium frequency function generator

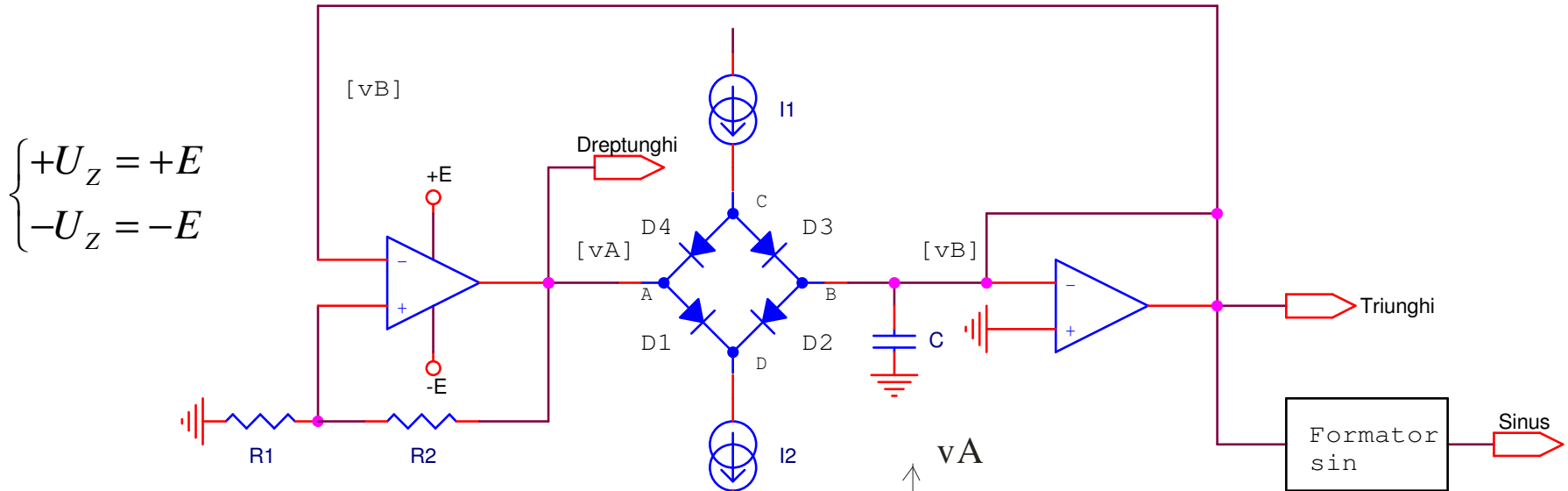


$$U_{P+} = \frac{R_1 \cdot E}{R_1 + R_2} ; U_{P-} = -\frac{R_1 \cdot E}{R_1 + R_2}$$

$$v_A = +E \Rightarrow \text{cmd } I_1 (D_{1,3} \text{ on}, D_{2,4} \text{ off})$$

$$v_A = -E \Rightarrow \text{cmd } I_2 (D_{1,3} \text{ off}, D_{2,4} \text{ on})$$
 
$$T = T_a + T_b = 2U_P C \left(\frac{1}{I_1} + \frac{1}{I_2} \right)$$



EMI Ch 5 – Signal & Function Generator

- **Low-medium frequency function generator**
 - adjustable duty factor scheme


$$T_a = \frac{2U_P C}{I_1} = \frac{2U_P C}{kR_A E} (R_B + \alpha R)$$

$$T = T_a + T_b = 2U_P C \left(\frac{1}{I_1} + \frac{1}{I_2} \right) =$$

$$= 2U_P C \left(\frac{R_B + \alpha R}{kR_A E} + \frac{R_B + (1 - \alpha)R}{kR_A E} \right)$$


$$= \frac{2U_P C}{kR_A E} (2R_B + R) = ct$$
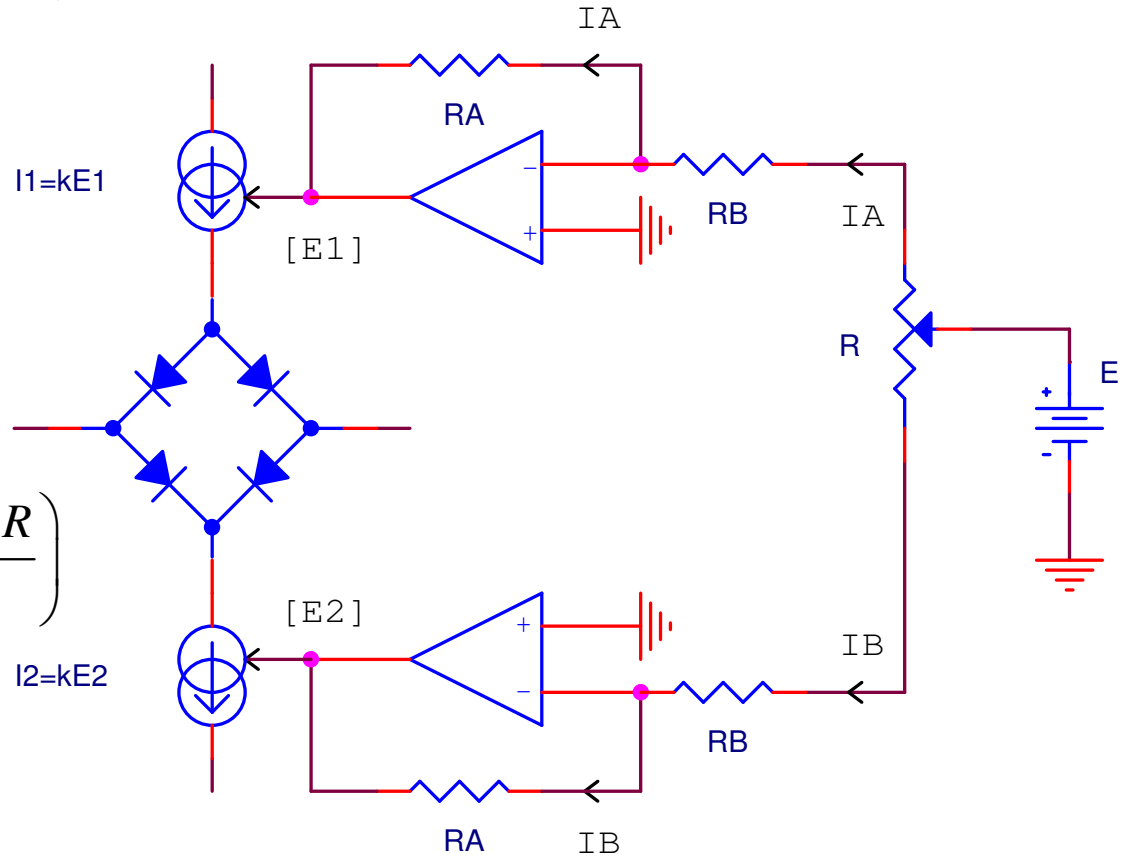
$$\eta = \frac{T_a}{T} = \frac{(R_B + \alpha R)}{(2R_B + R)} \sim \alpha$$



■ Low-medium frequency function generators

- sine shaper circuit

 

$$v_{IN} = v_T(\theta) = V_T \cdot \theta/90^\circ = V_T \cdot 4t/T \quad (V_T = \text{triangle waveform amplitude})$$

$$v_S(\theta) = V_S \sin \theta \quad (V_S = \text{sine amplitude})$$

$v_{out}(\theta)$ output signal approximates $v_S(\theta)$ using 4 segments/quadrant

Can obtain THD < 2%

■ Low-medium frequency function generators

• sine shaper circuit

$\Theta_2=30^\circ$

$\Theta_3=55^\circ$

$\Theta_4=75^\circ$

Slope comp. $m_1 \dots m_4$


Comp. R_i from m_i values

$$m_1 = \frac{\theta}{90}$$

$$m_2 = \frac{R_2}{R+R_2} \frac{\theta}{90} = \frac{R_2}{R_1+R_2} m_1 < m_1$$

$$m_3 = \frac{R_2 \parallel R_3}{R+R_2 \parallel R_3} m_1$$
 
$$m_4 = \frac{R_2 \parallel R_3 \parallel R_4}{R+R_2 \parallel R_3 \parallel R_4} m_1$$









EMI Ch 5 – Signal & Function Generator

■ Example: HP3314A




      - Freq. range 0.001Hz – 19.99MHz
- Digital adjustment of amplitude, frequency, offset, symmetry, phase
- AM, FM, modulation with external signal
- External trigger
- GATE mode
- Standard waveform + ARB (arbitrary)



EMI Ch 5 – Signal & Function Generator

■ Example: HP3314A – block scheme

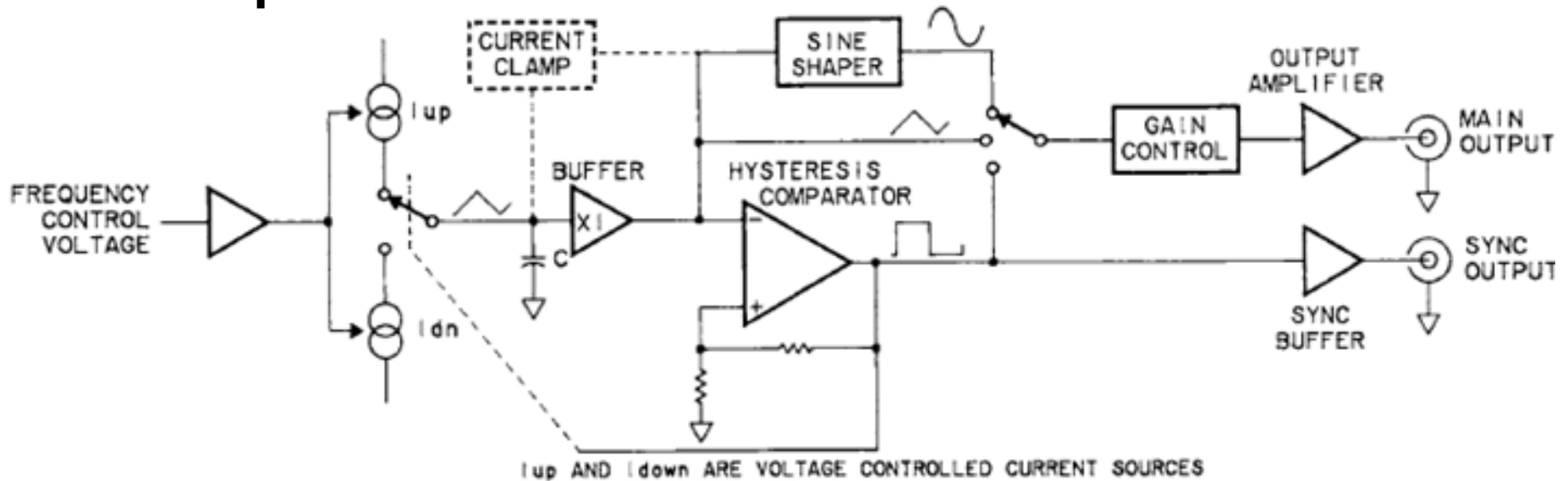


scale	Frequency range	C=	Buffer x1 / x10	I _{up} /I _{dn} x 10
1	0.001-2Hz	2.77uF	x10	da
2	1Hz-20Hz	2.77uF	x10	nu
3	10Hz-200Hz	2.77uF	x1	nu
4	100Hz-2KHz	277nF	x1	nu
5	1-20KHz	27.7nF	x1	nu
6	10-200KHz	2777pF	x1	nu
7	0.1-2MHz	277pF	x1	nu
8	1MHz-19.99MHz	27.7pF	x1	nu

■ Phase Loop Lock (PLL)

Negative feedback control system where f_{out} tracks f_{in} and rising edges of input signal align to rising edges of output signal;

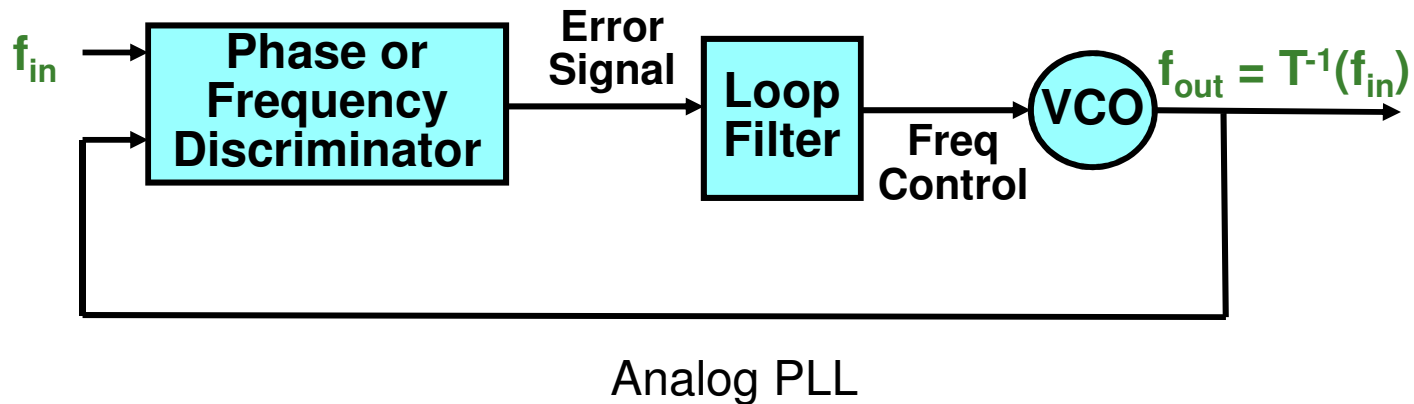- PLL types:
 - analog (linear) PLL;
 - digital PLL;
 - all digital PLL;



■ **Loop classification**

Loop Order (1st, 2nd, etc.)

Phase vs Frequency Lock

PLL Lower Near in Phase Noise

PLL: Loop Noise Converted to White Phase Noise

FLL: Loop Noise Converted to White Frequency

Noise

FLL Settles Faster

Implementation

Analog Loops

Analog Phase Discriminator

Digital Phase Discriminator

Digital Loop (Filter)

Phase/Frequency Error Quantization

Continuous (or Near Continuous)

Bang-Bang (Sign of Error)

■ Analog PLL principle

- Components:
 - Phase or frequency discriminator (PFD) – multiplier (analog inputs)
 - Loop filter
 - Voltage controlled oscillator (VCO)



• PFD

$$s_{in}(t) = A_1 \sin(\omega_{in} t + \phi_{in})$$

$$s_{osc}(t) = A_2 \cos(\omega_{in} t + \phi_{osc})$$

$$s_e(t) = s_{in}(t) s_{osc}(t)$$
  
$$= K_m \frac{A_1 A_2}{2} \sin(\phi_{in} - \phi_{osc}) + K_m \frac{A_1 A_2}{2} \sin(2\omega_{in} t + \phi_{in} + \phi_{osc})$$



- Loop Filter – Low pass filter (LPF)

$$s_{contr}(t) = \mathcal{F}^{-1}\{H_{LPF}(f) \cdot S_e(f)\} = K_{LPF} K_m \frac{A_1 A_2}{2} \sin(\phi_{in} - \phi_{osc})$$

■ Analog PLL principle

- VCO – oscillator with output frequency controlled by input voltage

$$f_{osc} = f_0 + K_O \cdot s_{contr}(t)$$

$$\phi_{osc}(t) = 2\pi \int_0^t (f_{osc}(\tau) - f_0) d\tau$$


$$= 2\pi K_O \cdot \int_0^t s_{contr}(\tau) d\tau = 2\pi K_O t \cdot s_{contr}(t)$$

$$s_{contr}(t) = K_{LPF} K_m \frac{A_1 A_2}{2} \sin(\phi_{in} - 2\pi K_O t \cdot s_{contr}(t))$$

The equation of $s_{contr}(t)$ can be linearized by making following assumption

For small θ , $\theta \approx \sin(\theta)$
 
$$s_{contr}(t) \approx K_{LPF} K_m \frac{A_1 A_2}{2} (\phi_{in}(t) - 2\pi K_O t \cdot s_{contr}(t))$$



■ Analog PLL principle

• Transfer function $H_{PLL}(s)$


- K_m – gain of PFD;
- K_{LPF} – gain of loop filter (LPF);
- K_0 – gain of VCO;

$$s_{out}(t) = A_0 \cos \left(2\pi f_0 t + K_0 \int_{t_1}^{t_2} s_{contr}(t) d\tau \right)$$

$$H(s) = \frac{P_f(s)}{1 - P_f(s)P_b(s)} \quad \left. \begin{array}{l} P_f(s) = \frac{1}{s} K_m K_{LPF} K_0 H_{LPF}(s) \\ P_b(s) = 1 \end{array} \right\} \Rightarrow H_{PLL}(s) = \frac{K \cdot H_{LPF}(s)}{s + K \cdot H_{LPF}(s)}$$

In case of $H_{LPF}(s) = \frac{1+s\tau_1}{1+s\tau_2} \Rightarrow H_{PLL}(s) = \frac{K(1+s\tau_1)}{\tau_2 s^2 + K(1+s\tau_1) + K}$
 
$$H_{PLL}(s) = \frac{\omega_n^2 + 2s\xi\omega_n}{s^2 + 2s\xi\omega_n + \omega_n^2} \quad ; \quad \omega_n = \sqrt{\frac{K}{\tau_1}} \quad ; \quad \text{damp factor } \xi = \frac{\omega_n \tau_2}{2}$$



■ Digital Phase Loop Lock (PLL)

- PLL can acts as:

Operation Inverter

VCO output f_{out} goes through frequency translation $T(f_{out})$


Phase or Frequency Discriminator compares f_{in} to $T(f_{out})$ and generates error signal

Through Loop Filter and VCO frequency control, error signal driven to 0 so

$f_{in} = T(f_{out})$; thus VCO output is inverse of T $f_{out} = T^{-1}(f_{in})$

Tracking Filter

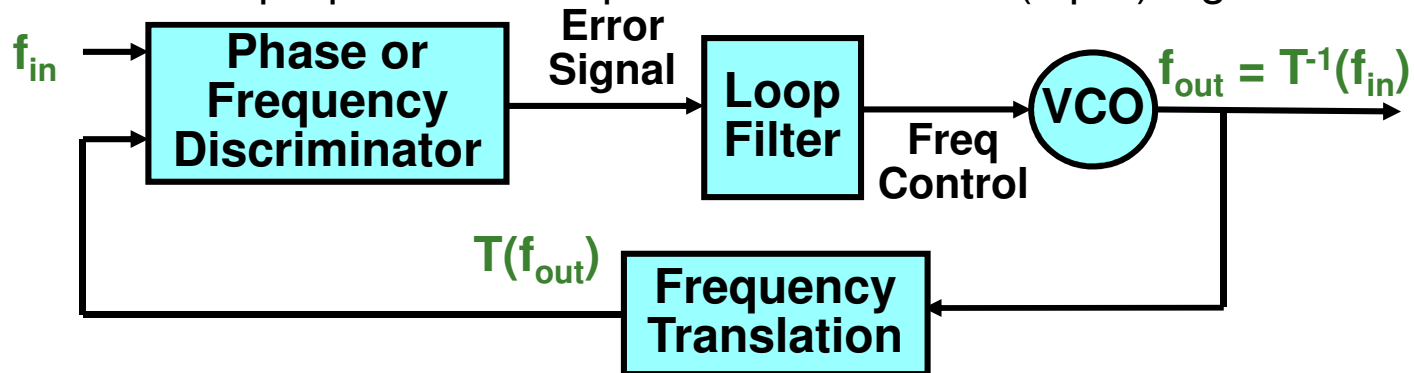Uses bandwidth properties of loop to filter reference (input) signal



Digital PLL


■ Digital Phase Loop Lock (PLL)

• Digital PD

Inputs – digital signals

Function interval ϕ $[-\pi/2, +\pi/2]$

 
Functioning condition $f_{in} \approx f_{osc}$



LPF selects DC component of XOR


$$V_d = V_a - V_b$$
 
$$\begin{cases} V_d = \min \Rightarrow \Delta\phi = 0 & (V_a \text{ and } V_b \text{ in phase}) \\ V_d = 0 \Rightarrow \Delta\phi = \pi/2 & (V_a \text{ and } V_b \text{ in quadrature}) \\ V_d = \max \Rightarrow \Delta\phi = \pi & (V_a \text{ and } V_b \text{ in anti-phase}) \end{cases}$$



■ Digital Phase Loop Lock (PLL)

• Digital PFD

 


PFD = Phase-Frequency Discriminator

- Tracking phase range $-2\pi \dots 2\pi$ (even $f_{in} \neq f_{out}$)
- V_U = UP (increase f_{osc} from VCO output)
- V_D = DOWN (decrease f_{osc})
- Z = LPF input and then command to VCO

■ Digital PFD

 
- waveform for $f_{in} = f_{out}$ and $\varphi_{in} \neq \varphi_{out}$



- First pulse (active rising slope) sets corresponding D flip-flop (exp. $V_i \rightarrow V_u$ on)
- Second pulse sets the other D flip-flop (exp. $V_o \rightarrow V_d$ on)
- AND gate resets both D flip-flop: V_u, V_d off (on time of V_d neglected)
- Case V_{out} slower than V_{in} ; V_{in} sets the first D flip-flop, $V_u > V_d \rightarrow$ “UP”, VCO will be “accelerated” and V_{out} will “catch up” V_{in}

■ Digital PFD


- waveform for $f_{in} \neq f_{out}$

 

- $f_{in} > f_{out}$, $V_u > V_d \rightarrow$ “UP” ,
- VCO will be “accelerated” and V_{out} will “catch-up” V_{in}

■ Digital PFD

 - waveform for $f_{in} \neq f_{out}$ and a periodic signals



- Mean of $f_{in} < \text{mean of } f_{out}$, $V_u < V_d \rightarrow \text{“DOWN”}$,
- VCO will be “slowed down” and V_{in} will “catch-up” V_{out}

■ Digital Phase Loop Lock (PLL)

- PLL can acts as:

Operation Inverter

VCO output f_{out} goes through frequency translation $T(f_{out})$


Phase or Frequency Discriminator compares f_{in} to $T(f_{out})$ and generates error signal

Through Loop Filter and VCO frequency control, error signal driven to 0 so

$f_{in} = T(f_{out})$; thus VCO output is inverse of T $f_{out} = T^{-1}(f_{in})$

Tracking Filter

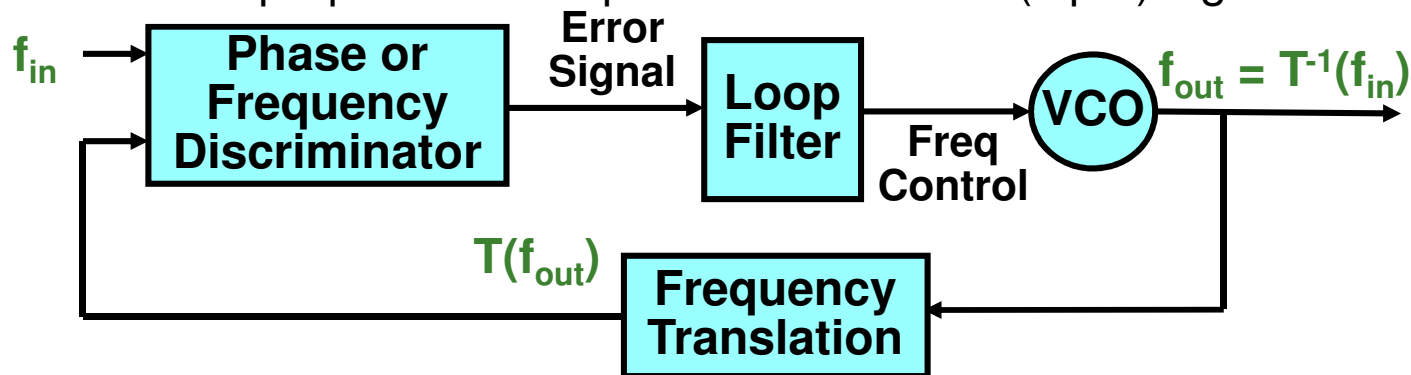Uses bandwidth properties of loop to filter reference (input) signal



Digital PLL

■ Digital Phase Loop Lock (PLL)

- PLL can acts as:

Operation Inverter

VCO output f_{out} goes through frequency translation $T(f_{out})$


Phase or Frequency Discriminator compares f_{in} to $T(f_{out})$ and generates error signal

Through Loop Filter and VCO frequency control, error signal driven to 0 so

$f_{in} = T(f_{out})$; thus VCO output is inverse of T $f_{out} = T^{-1}(f_{in})$

Tracking Filter

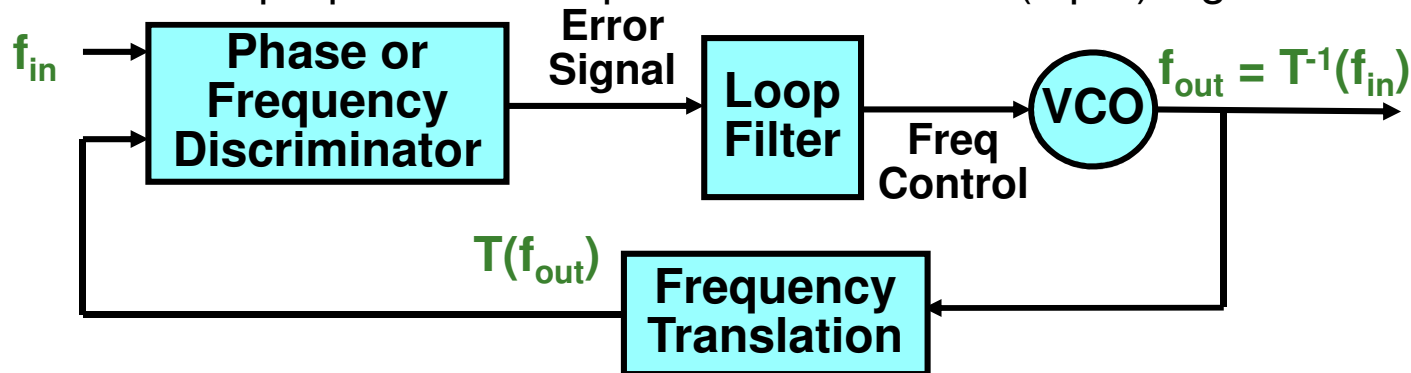
Uses bandwidth properties of loop to filter reference (input) signal



Digital PLL


■ Direct Digital Synthesizer (DDS)

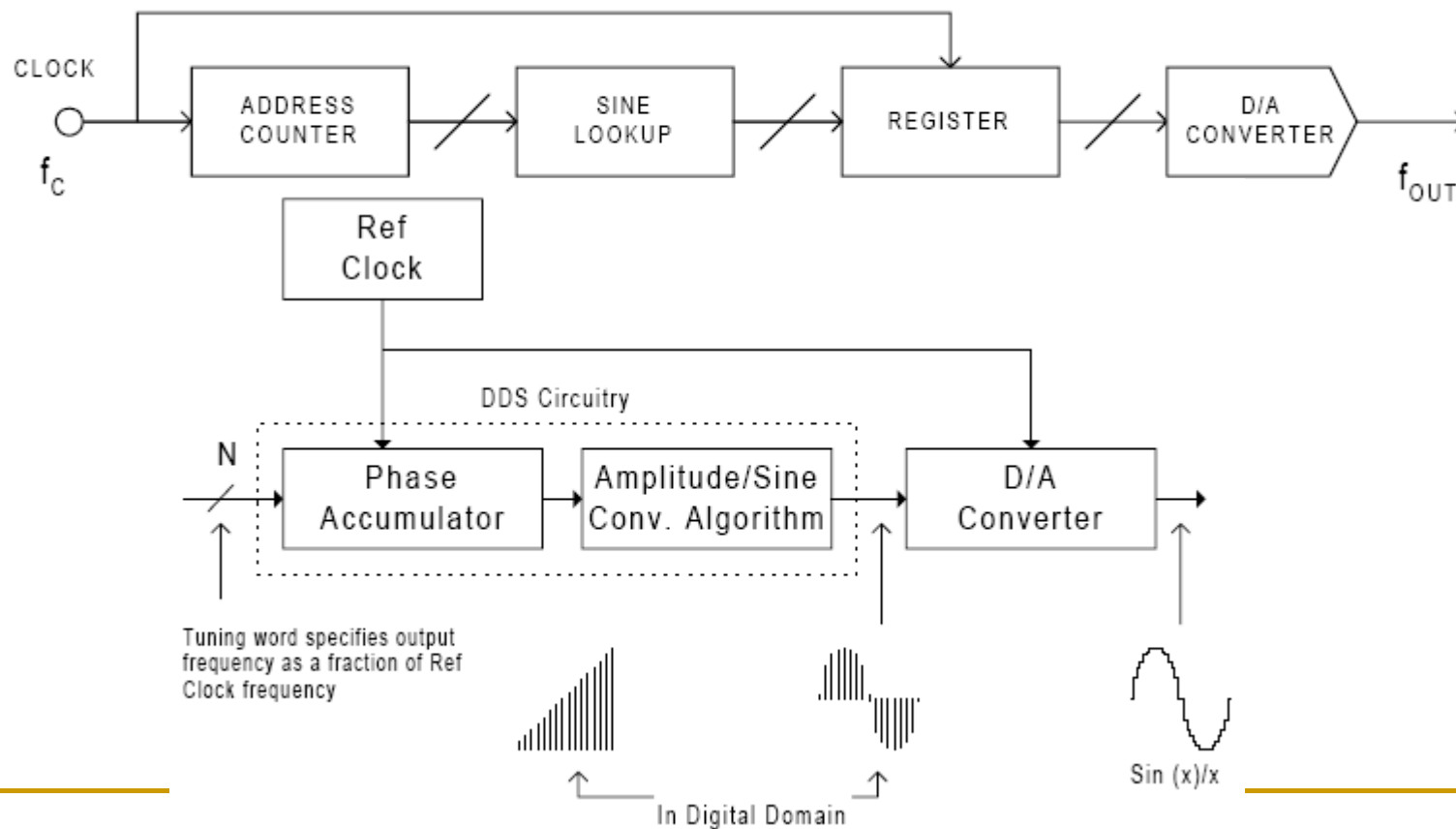- a technique that uses digital data processing to generate a frequency/phase-tunable output signal referenced to a fixed-frequency precision clock source




■ Direct Digital Synthesizer (DDS)

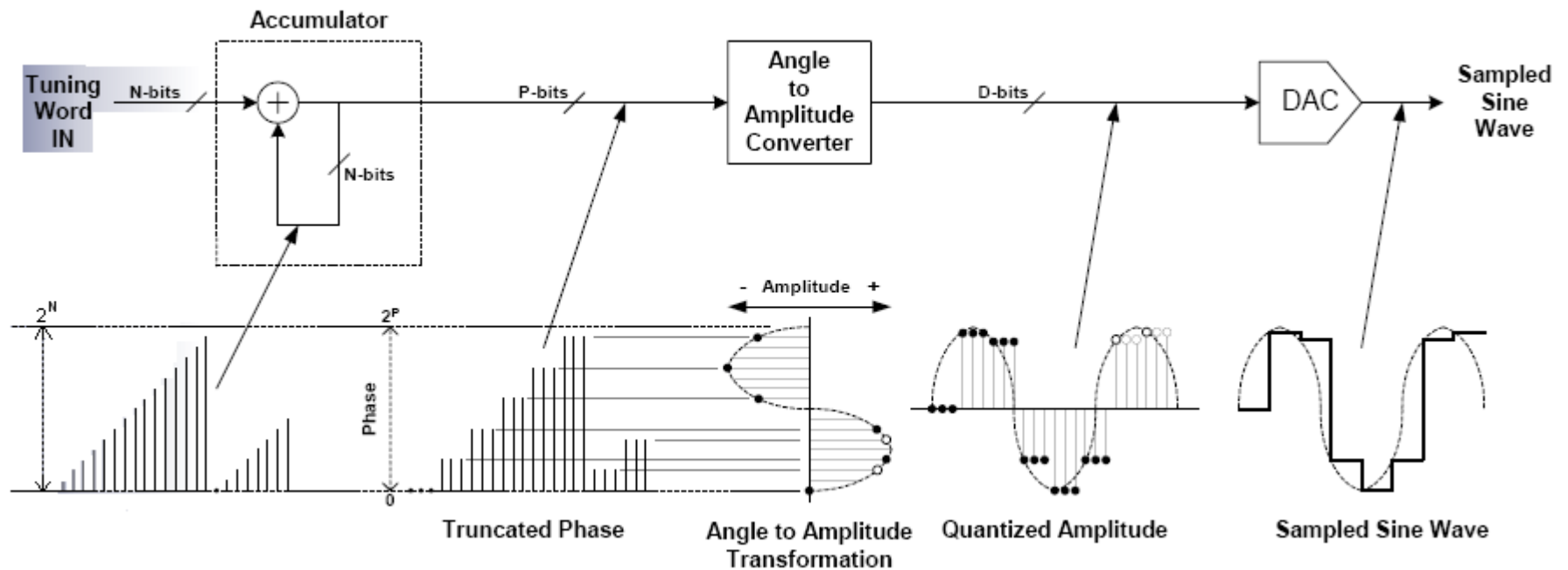- a technique that uses digital data processing to generate a frequency/phase-tunable output signal referenced to a fixed-frequency precision clock source
-




■ Direct Digital Synthesizer (DDS)

- Frequency Shift Keying

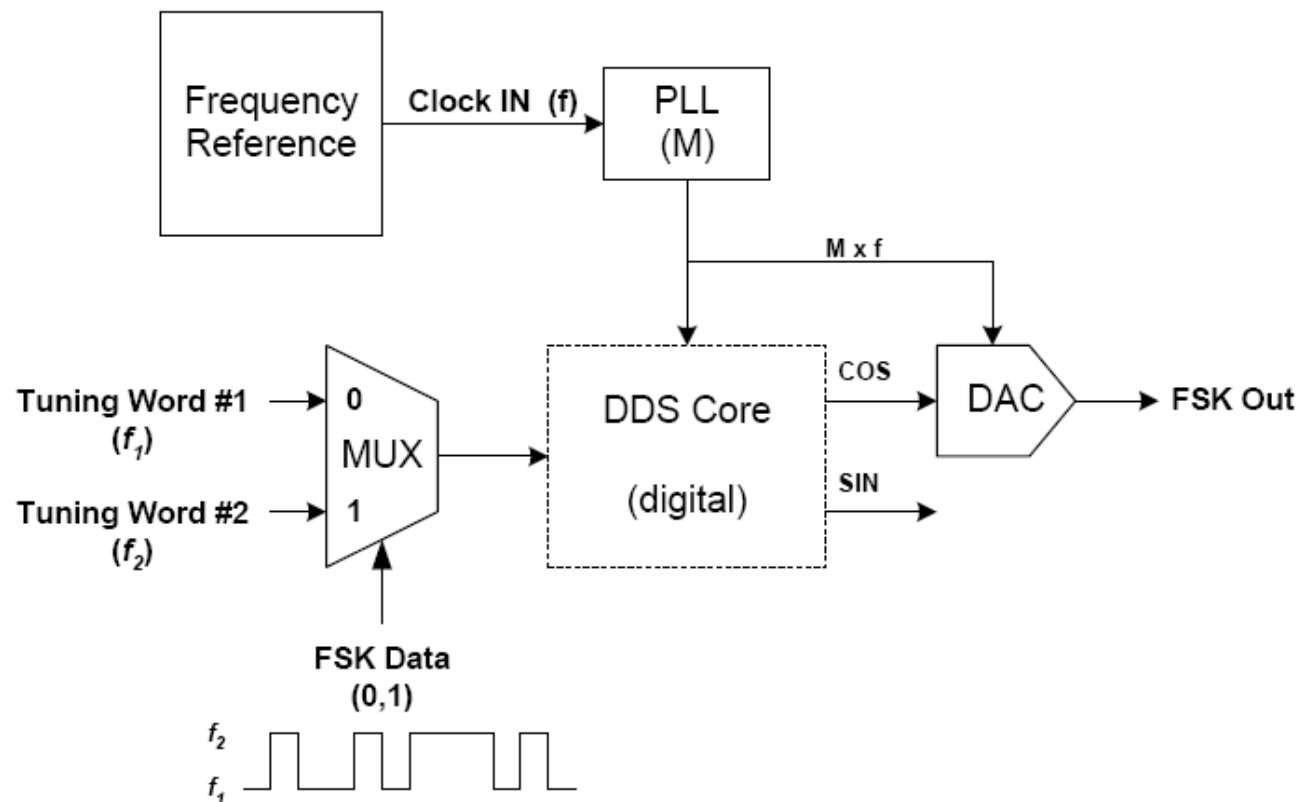


■ Direct Digital Synthesizer (DDS)

- Phase Shift Keying

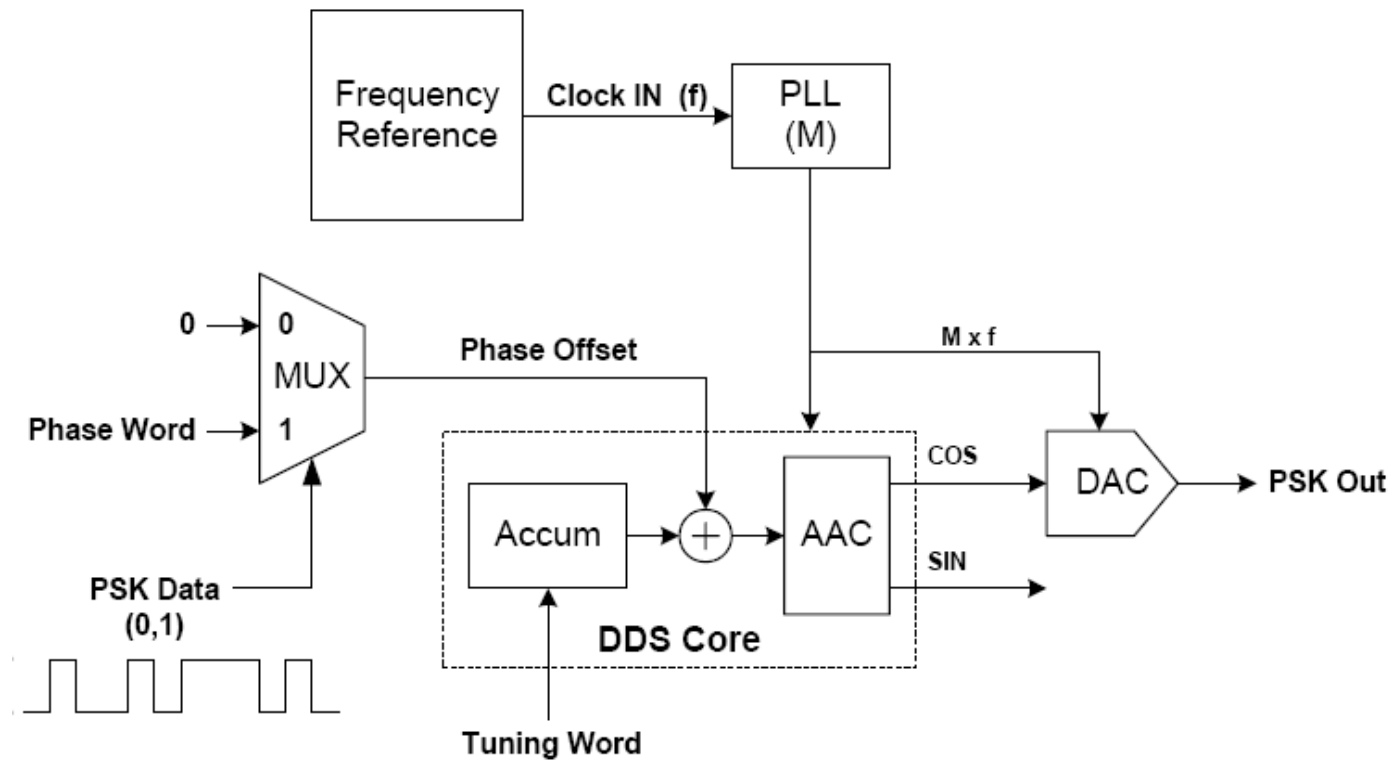


■ Direct Digital Synthesizer (DDS)

- Quadrature amplitude modulation

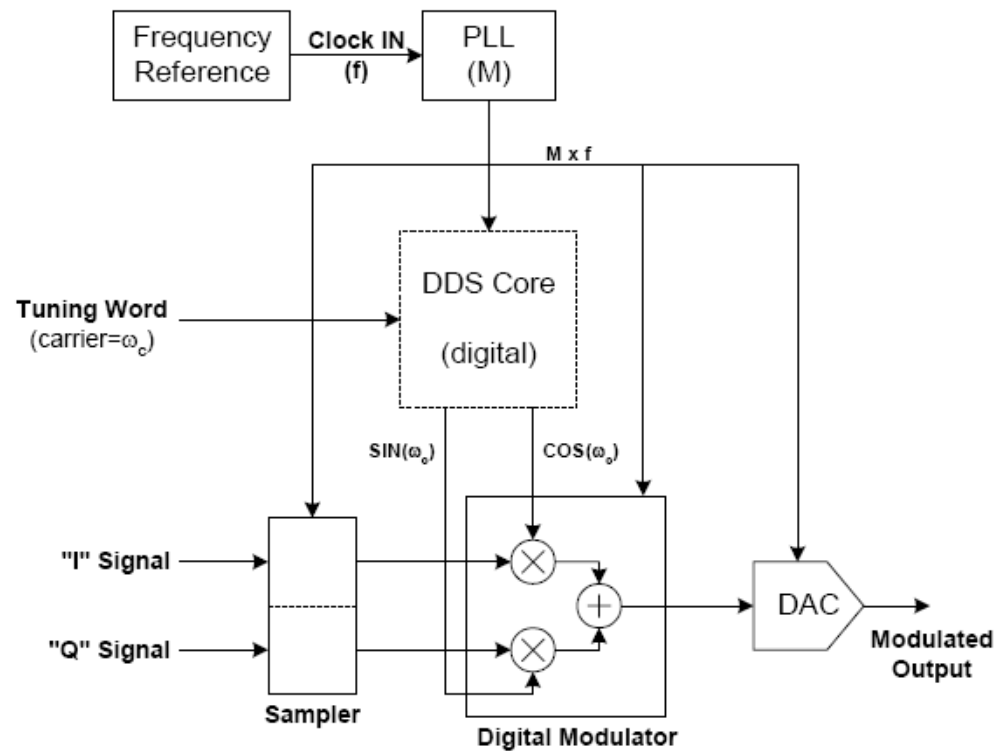

■ Direct Digital Synthesizer (DDS)

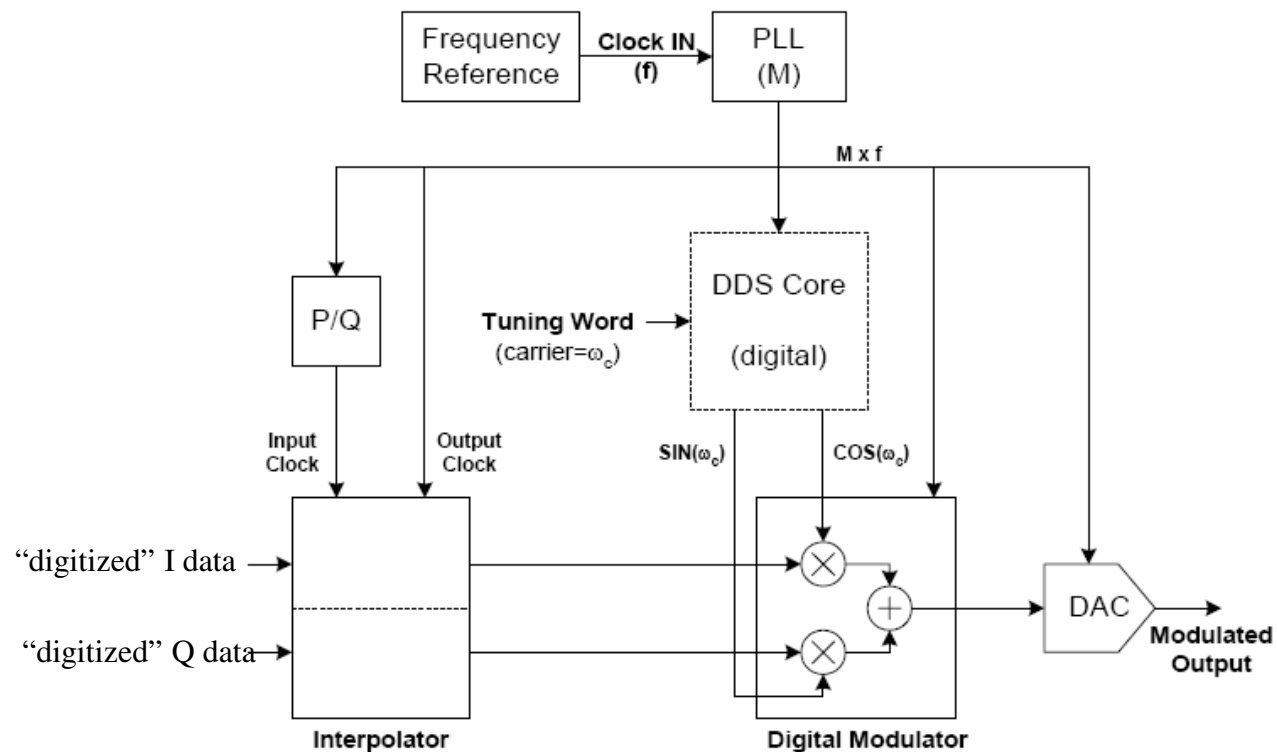- Quadrature Up-Converter amplitude modulation



■ Direct Digital Synthesizer (DDS)

- Chirp modulation

